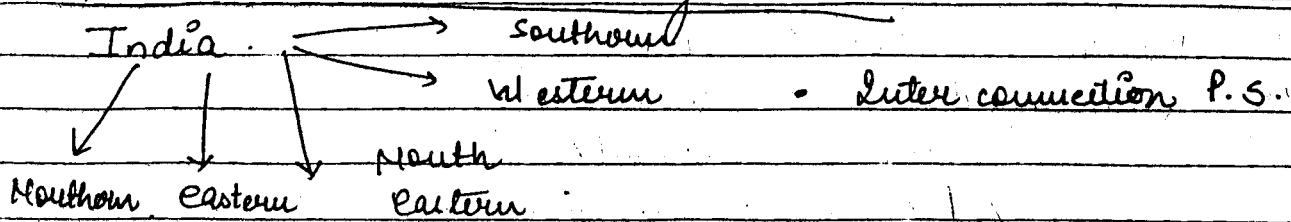


Power System -

Power systems ?

1. Power system Generation
 2. Transmission and distribution
 - ↳ Tx-line constants
 - ↳ Tx-line performance.
 - Wave nature
 - Surges
 - Voltage control
 - VG cable
 - Insulators.
 - corona
 - Distribution Sy
 - HVDC
 3. Fault Analysis → Geometrical component
 - sequence n/w
 - symmetrical fault
 - unsymmetrical fault
 - Z bus based fault
 4. P.S. stability → steady state Stability
 Transient stability
 5. Protection
 6. load flow
 7. Economic Dispatch (IES)
- Weightage → (8-10) marks
- Books : JB Gupta
 CL Madhava.


Introduction to Power system :-



* India has 5 regional grids which are interconnected with each other in order to supply power from energy surplus areas to energy deficit area.

* In interconnected P.S there is more efficient utilization of energy but at the same time there is a risk of fault propagation from one part of P.S to the other.

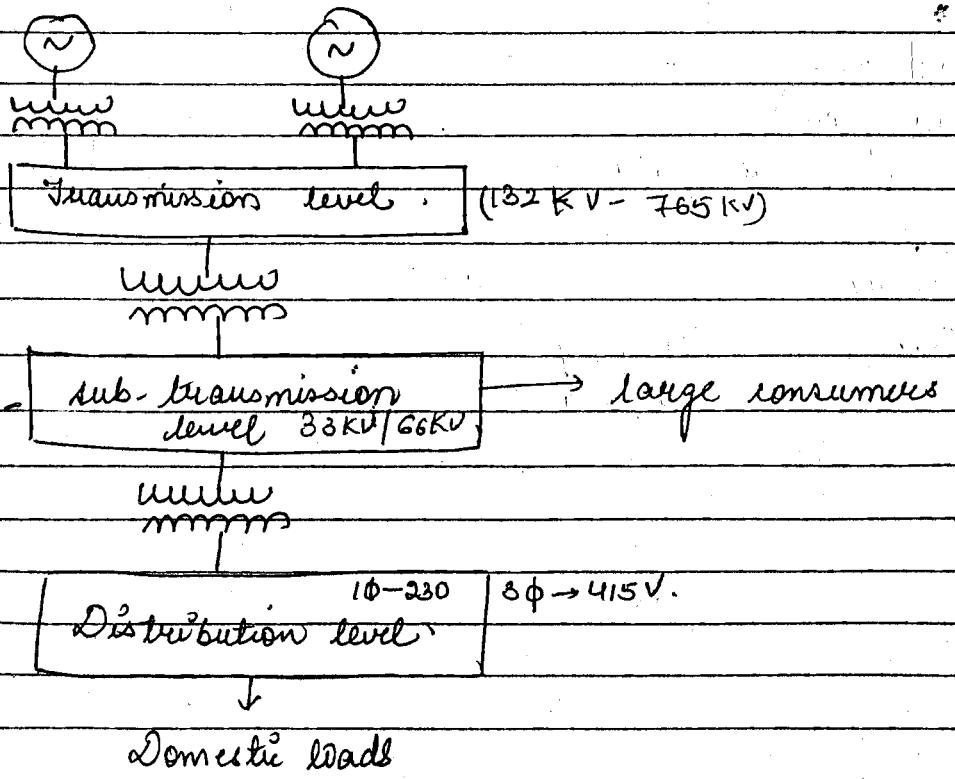* So, we realize the concept of smart grid in which load scheduling is automatic but there must be effective protection by developing communication b/w the substations.




Objectives of power system?

- ⇒ cost of per unit energy should be minimized. (per kWh).
 - ↳ economic generation
 - ↳ economic load dispatch \Rightarrow (load sharing)
 - ↳ power generation method.
- ⇒ effective protection against fault.
 - ↳ fault analysis
 - ↳ switch gear and protection.
- ⇒ rated v/f and frequency must be supplied to consumer.
 - ↳ automatic v/f control
 - ↳ load freq. control. \rightarrow speed governor.
- ⇒ Power system must be stable.
 - ↳ Power sys stability
- ⇒ reliable power supply to consumer.
 - ↳ Transmission and distribution


Per unit System?

single line diagram:

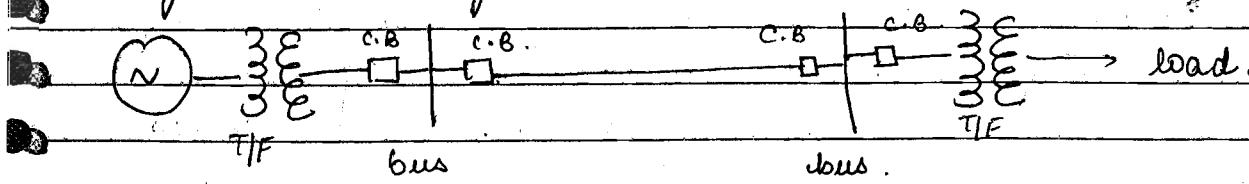


Actual eqt?

1. Generator.

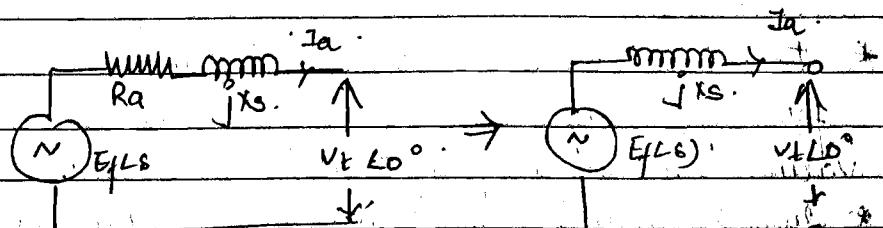


2. Transformer.

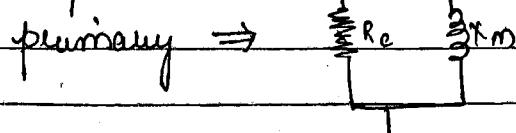


\Rightarrow shunt branch ignored.

secondary?

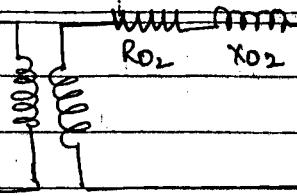


3. Transmission line

short transmission line.

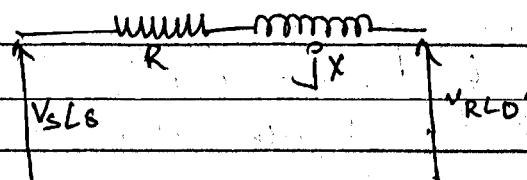

- * the loads are generally modelled as constant power load where the real and reactive powers of the load is specified.


Overall circuit

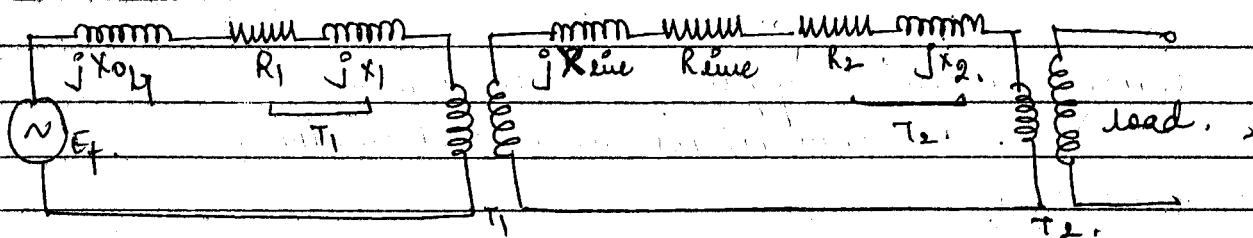

The eq. circuit of P.S. is complicated due to multiple component being present but single line diagram is a specified representation which is easily readable

- * to analyze the given circuit, we need 3 KVL eq. for 3 loops and hence analysis in absolute values is complicated.

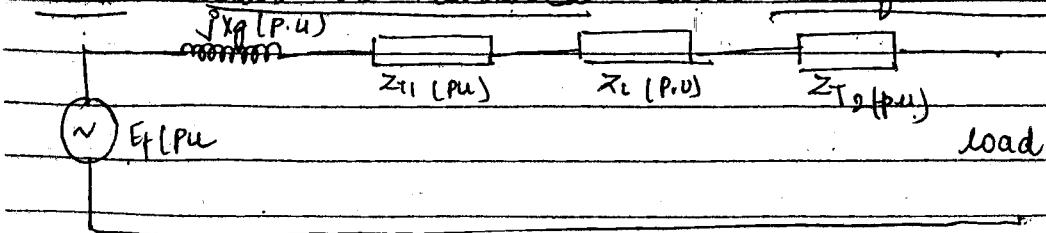
* In per unit system, the pu values of all quantities are same on both sides of Trans. so the turns ratio can be removed and no of KVL eq. reduces.



Q To convert a P.S in per unit? -

we must use a universal base so that results are consistent with the actual values.

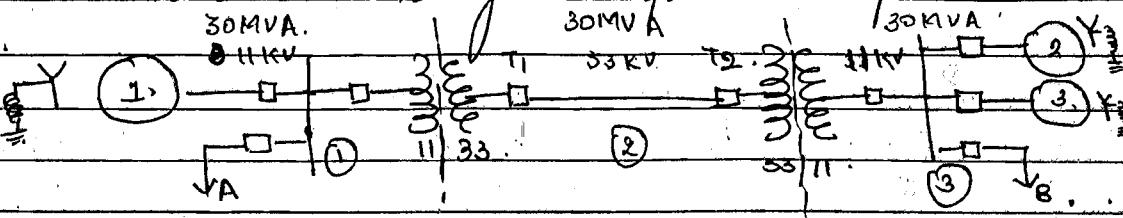Q Draw the reactance diagram for the p.s shown in fig.



G₁ :- 30 MVA, 11 kV, $X'' = 1.6 \Omega$.

G₂ :- 15 MVA, 33 kV, $X'' = 1.2 \Omega$.

G₃ :- 25 MVA, 11 kV, $X'' = 0.56 \Omega$.

T₁, T₂ :- 15 MVA, 33/11 kV. $X = 15.2 \Omega/\phi$ on HV side.

Trans. ratio $\rightarrow 20.5 \Omega/\phi$.

Base = 30 MVA [power base will be same].

* While choosing the base, kVA base remain same for the entire p.s but we only choose 1/g base for 1 section and then scaled it on the basis of turns ratio : see transformation ratio of X-mu.

$$X_{pu} = \frac{1.6}{(11^2/30)} = 0.396$$


$$X_{T1}(pu) = \frac{15.2}{(33^2/30)} = 0.4187$$

$$X_{Tline} = \frac{20.5}{33^2/30} = 0.5647$$


$$X_{T2}(pu) = \frac{15.2}{33^2/30} = 0.418$$

$$X_d = \frac{1.2}{(11^2/30)} = 0.297$$
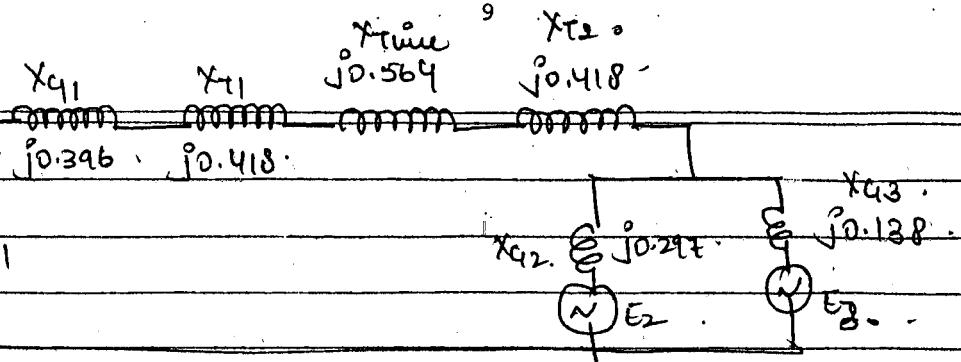
$$\delta = \frac{0.56}{11^2/30} = 0.138$$



a. Draw the impedance diagram

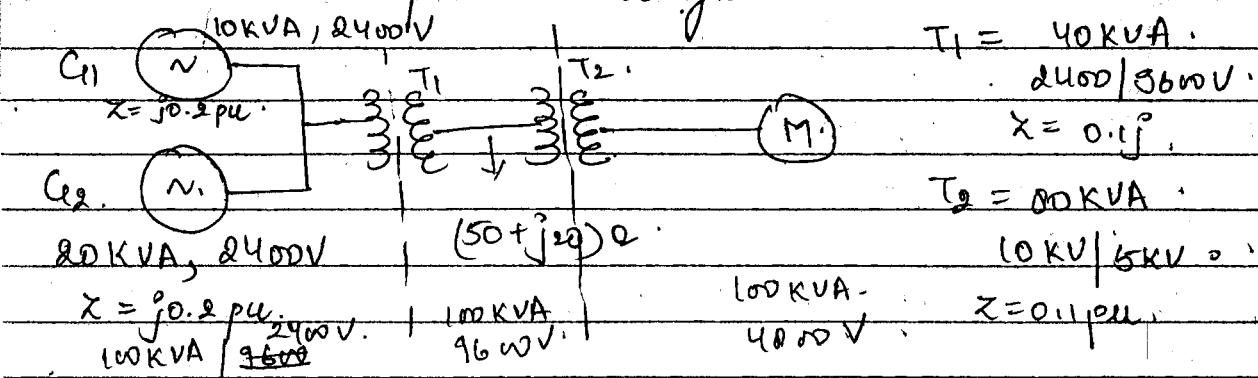

Choose base for Generator 1 as $M = 25 \text{ KVA}, 4 \text{ KV}$
 $2400 \text{ V} | 100 \text{ KVA}$

$$Z = j0.3 \text{ pu.}$$

Given Base = 100 KVA, 2400V

$$G_1 = j0.2 \times \left(\frac{100}{10}\right) \times \frac{2400}{2400} = 2j$$


$$G_2 = j0.2 \times \left(\frac{100}{20}\right) \times 7 = j1$$

$$T_1 = j0.1 \times \left(\frac{100}{40}\right) = 0.25j$$

$$Z_L = \frac{50 + 20j}{\frac{2400^2}{100 \times 10^3}} \Rightarrow 0.054 + j0.217$$

$$X_T 2 = j0.1 \times \left(\frac{100}{80}\right) \times \left|\frac{5000}{4800}\right|^2 = j0.135$$
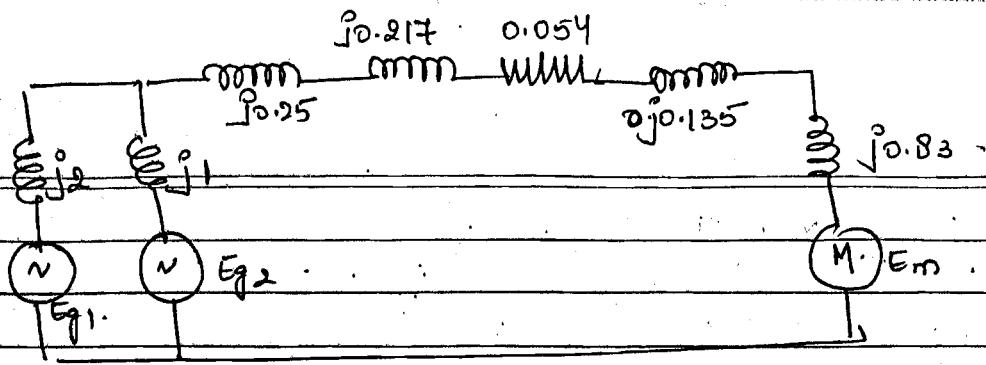
$$X_M = 0.3j \times \left(\frac{100}{25}\right) \times \left(\frac{4000}{4800}\right)^2 = 0.833j$$



A 3-bus system is given as shown in fig.

$G_1 = 50 \text{ MVA}, 13.8 \text{ KV}, X'' = 0.15 \text{ pu}$

$G_2 = 40 \text{ MVA}, 13.2 \text{ KV}, X'' = 0.2 \text{ pu}$

$G_3 = 30 \text{ MVA}, 11 \text{ KV}, X'' = 0.25 \text{ pu}$

$T-1 = 45 \text{ MVA}, 11 \text{ KV} / \Delta / (110 \text{ KV}) \quad X = 0.1 \text{ pu}$


$T-2 = 25 \text{ MVA}, 12.5 \text{ KV} (\Delta) / 115 \text{ KV} (Y) \quad X = 0.15 \text{ pu}$

$T-3 = 40 \text{ MVA}, 12.5 \text{ KV} (\Delta) / 115 \text{ KV } Y \quad X = 0.1 \text{ pu}$

Line X'' are shown in fig

Choose base values as 50 MVA, and 13.8 KV on.

G_1 side.

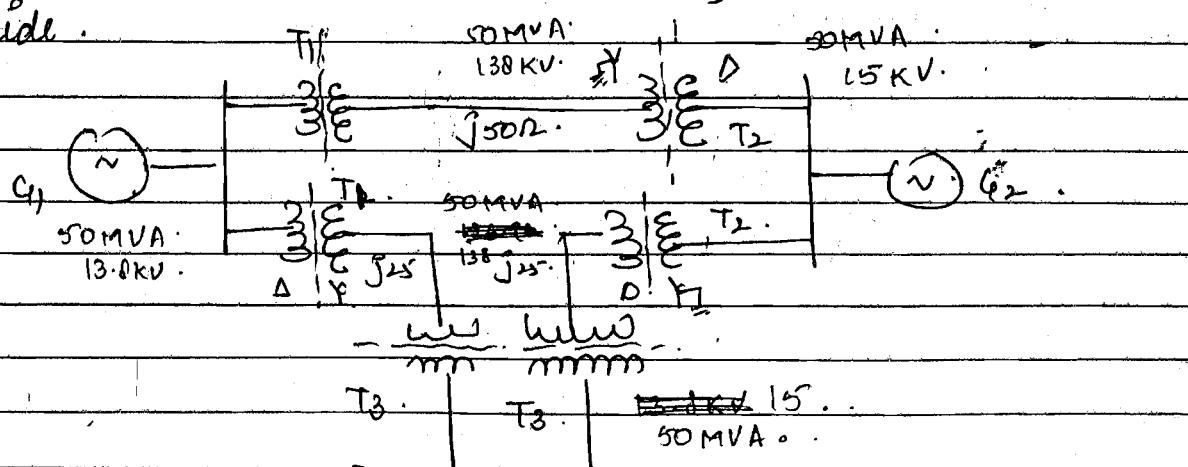

$$G_1 = 0.15 \times \left(\frac{50}{50}\right) \times \left(\frac{13.8}{13.8}\right)^2 \times 3002 = 0.15 \text{ p.u.}$$

$$G_2 = 0.2 \times \left(\frac{50}{40}\right) \times \left(\frac{13.2}{13.2}\right)^2 = 0.1936 \text{ p.u.}$$

$$G_3 = 0.25 \times \left(\frac{50}{30}\right) \times \left(\frac{11}{11}\right)^2 = 0.2240 \text{ p.u.}$$


$$T_1 = 0.1 \times \left(\frac{50}{45} \right) \times \left(\frac{11}{13.8} \right)^2 = 0.0705$$

$$T_2 = 0.15 \times \left(\frac{50}{25} \right) \times \left(\frac{12.5}{15} \right)^2 = 0.208$$

$$T_3 = 0.1 \times \left(\frac{50}{40} \right) \times \left(\frac{12.5}{15} \right)^2 = 0.086 \cdot 0.0806$$

$$T_4 = \frac{50}{(138^2/50)} = 0.131$$

$$T_2 = T_3 = 0.065$$

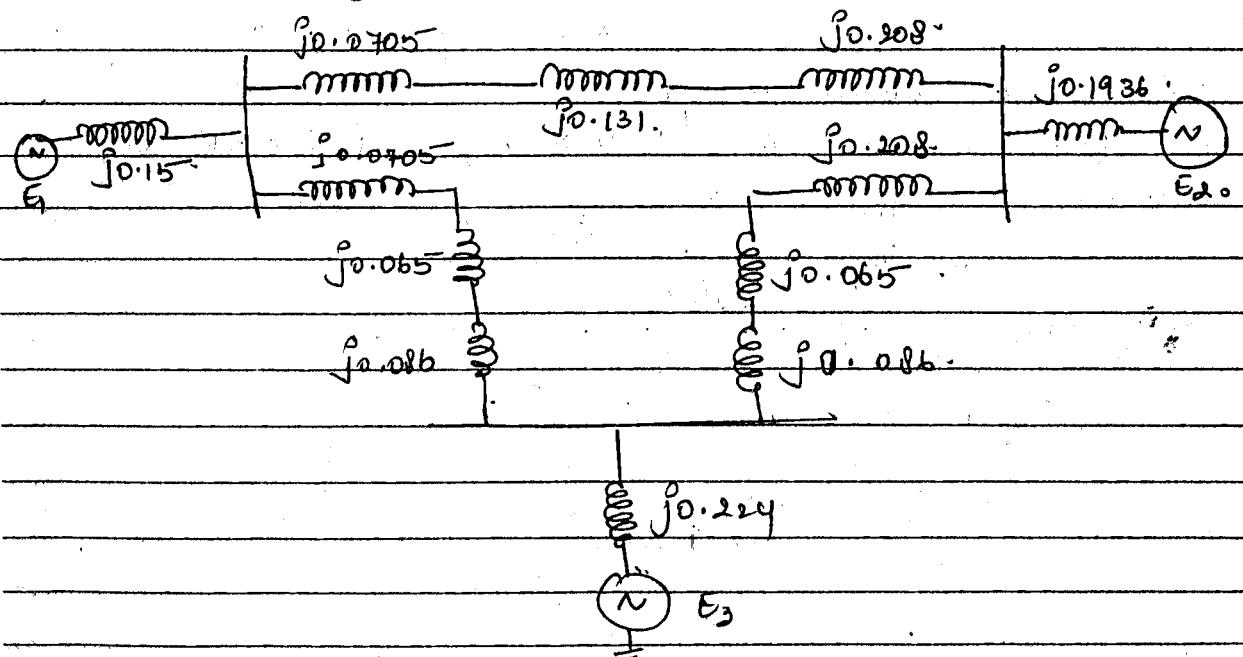

A 220 MVA, 66 KV, 3φ generator has $x_{\text{sub}}^1 = 30\%$, the 4 motors connected to 3 Motors through a Y-mission line and transformers as shown in fig, the motors have rated input of 60 MVA, 40 MVA, 100 MVA with 40%, sub-transient reactance, the rating of X-motors are shown in fig. draw the reactance diagrams assuming X-mission line reactance = 100%.