

Diode Circuit - Part I

- ① ~~Diode with respect to DC source.~~
- ② ~~clipped circuit~~
- ③ ~~DC Power supply design~~
 - Rectifier + filter
 - + Voltage Regulator

④ Clamped


- ⑤ Small signal model of diode.
- Robert L. boykstead
 - millman Halkias
 - Sedra smith

Notes + R.K. Kannodia

Diode:


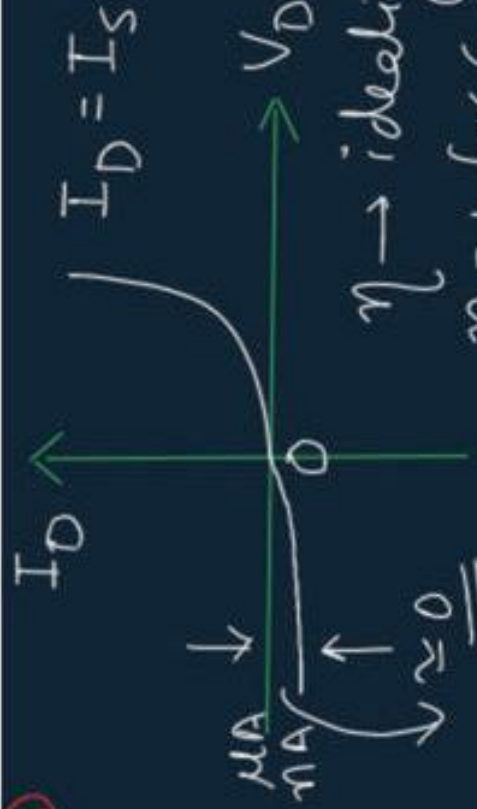
$$I_D = I_S (e^{\frac{V_D}{\eta V_T}} - 1)$$



$\eta \rightarrow$ ideality factor

$\eta = 1$ for Ge } generally
 $\eta = 2$ for Si }

$V_T \rightarrow$ Thermal voltage

$$V_T = \frac{T}{11,600}$$

$T \rightarrow$ kelvin

$I_S \rightarrow$ Reverse saturation current.


Diode Model: Diode application \rightarrow As a switch


① ideal diode:



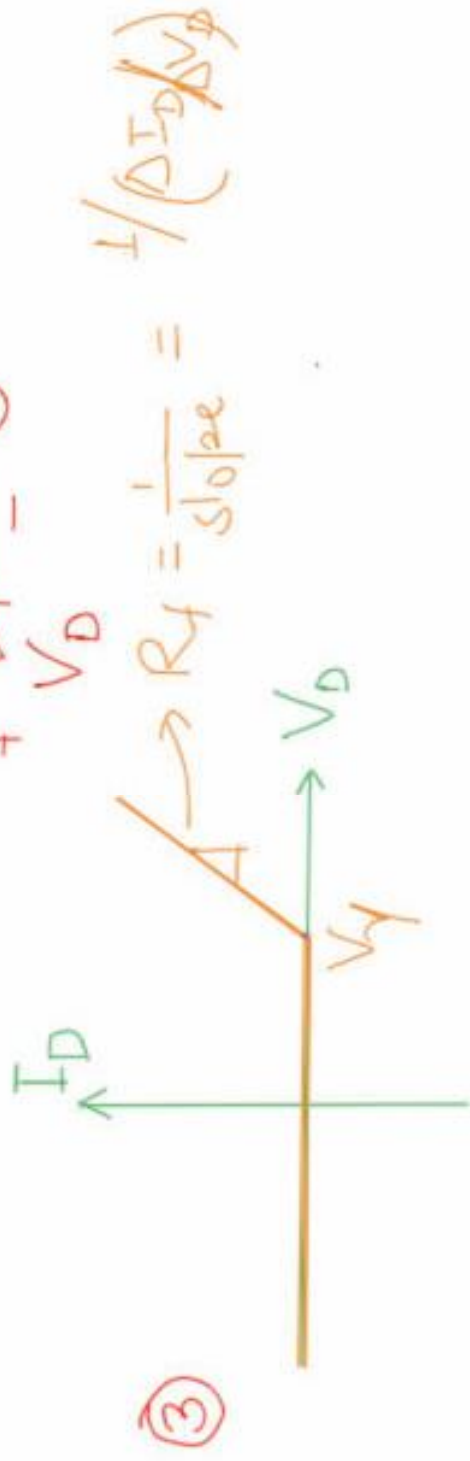$V_D < 0 : I_D = 0$;
 $V_D > 0 : I_D \neq 0$;





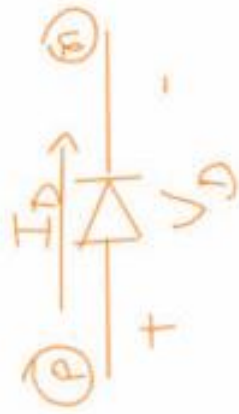

$$V_D < V_\gamma : I_D = 0 : \textcircled{P} \xrightarrow{\text{O.C.}} \textcircled{N} \text{ (OFF)}$$


$\xrightarrow{\text{O.A.}}$

$$V_D > V_\gamma : I_D \neq 0 : \textcircled{P} \text{ --- } V_\gamma \text{ --- } R_f \text{ --- } \textcircled{N} \text{ (ON)}$$

$+$ V_D $-$
 I_D



Q1

Find V_o

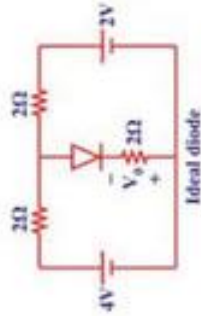

Procedure: (General)

#1 Let diode ON

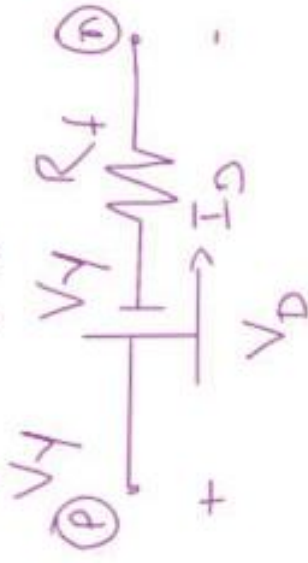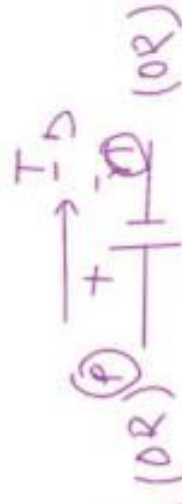

② find I_D

I_D (PTON) \rightarrow F.B (ON)

I_D (Ntop) \rightarrow R.B. (off)

(OR) 2nd way:

① Let diode off

$$\begin{array}{c} + \xrightarrow{I_D} \\ \text{---} \triangle \text{---} \\ V_D \end{array} \equiv \frac{\textcircled{P} + V_D - \textcircled{R}}{0.C} \xrightarrow{0A}$$

② If $V_D > 0$ (OR) $V_D > V_Y$ (OR) $V_D > V_Y$


: Diode ON ✓

if $V_D < 0$ (OR) $V_D < V_Y$ (OR) $V_D < V_Y$


: Diode off

Q.1

Find V_o

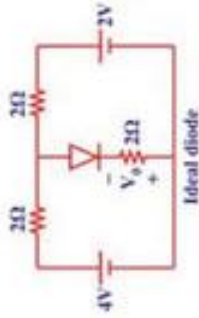

→ Let diode is (off):

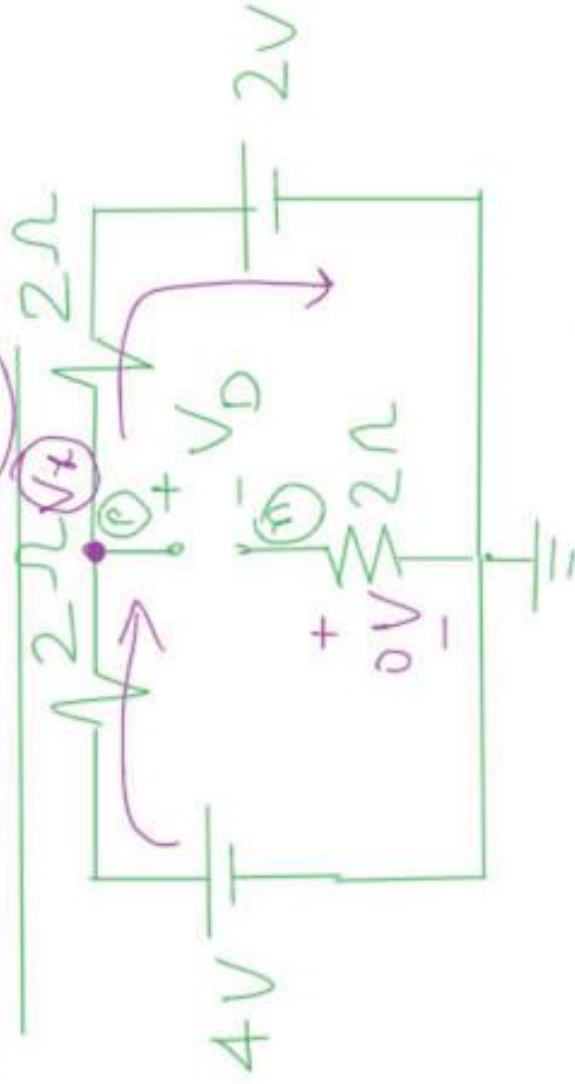

$$\frac{4 - V_x}{2}$$

$$= 0 + \frac{V_x - 2}{2}$$

\Rightarrow


$$6 = 2V_x$$

$$\boxed{V_x = 3V} = V_D$$

$V_D > 0$: (Diode ON)

Old Assumption is wrong.

Diode ON?

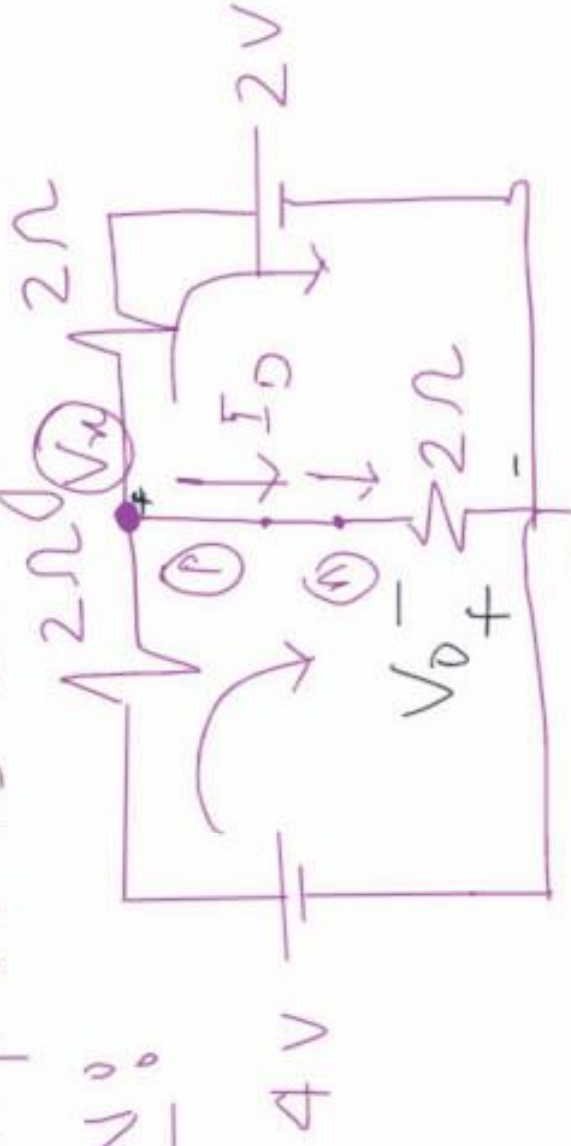

$$\frac{4 - V_x}{2} = \frac{V_x - 0}{2} + \frac{V_x - 2}{2} \Rightarrow 3V_x = 6$$

$$\boxed{V_x = 2V}$$

$$I_D = \frac{V_x - 0}{2} = 1A \text{ (PTON)}$$

Really diode is ON.

$$V_o = -V_x = \underline{\underline{-2V}} \text{ Ans.}$$