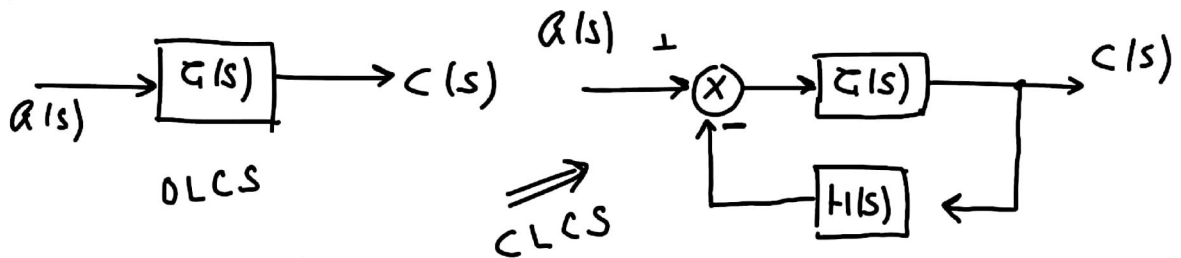


Introduction to Control Systems

Comprehensive Course on Control Systems - Part I

Aditya Kanwal • Lesson 1 • July 7, 2021

CONTROL SYSTEMS: -




Mathematical model. \Rightarrow M.M

\rightarrow Transfer function: - It is M.M of a physical system.

① It is the ratio of the LT of the o/p to the LT of the i/p with all initial conditions = 0.


~~Linear~~ TF is defined only for LTI.

$$T(s) = \frac{LT[o/p]}{LT[i/p]} \Big|_{\text{all ICs} = 0} = \frac{C(s)}{R(s)}$$

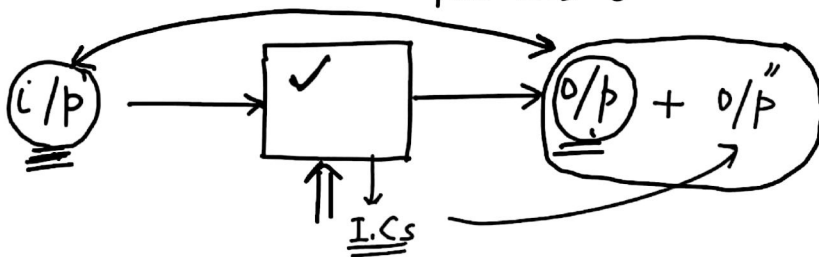

$$TF = \frac{LT[C(t)]}{LT[H(t)]} \neq LT \left[\frac{C(t)}{H(t)} \right]$$

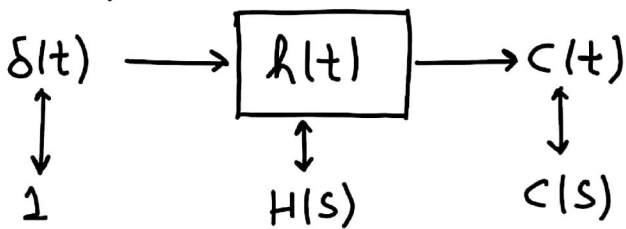2) TF can also be defined as the LT of the impulse response of the system. with all IC = 0



$$\underline{H(s)} = \frac{C(s)}{1} = \underline{C(s)}$$

$$C(t) = \delta(t) \otimes h(t)$$


$$C(t) = h(t)$$

$$\boxed{C(s) = H(s)}$$

$$\underline{h(t)} \rightarrow \boxed{h(t)} \rightarrow \underline{c(t)} \Rightarrow c(t) = h(t) \otimes h(t)$$

$$R(s) \rightarrow \boxed{H(s)} \rightarrow C(s) \Rightarrow C(s) = R(s) \cdot H(s)$$


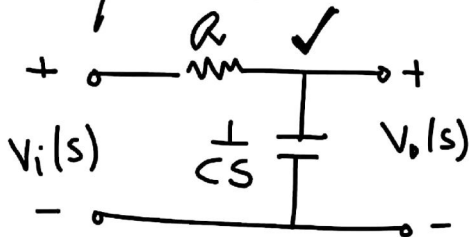
→ The order of the T.F of an electrical n/w is equal to the total no. of energy storage elements.



$$V_o(s) = \frac{V_i(s)}{R + \frac{1}{CS}} \cdot \frac{1}{CS}$$

$$\boxed{\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + RCS}}$$


Order - 1

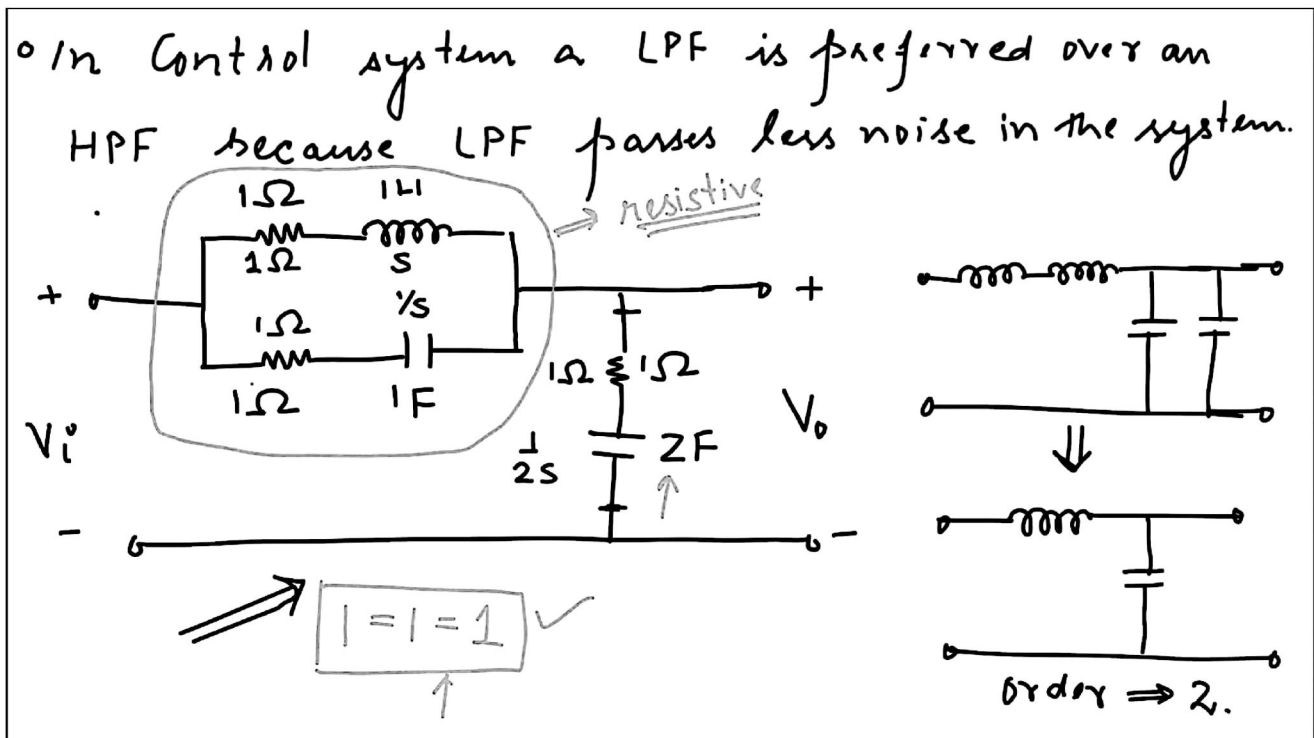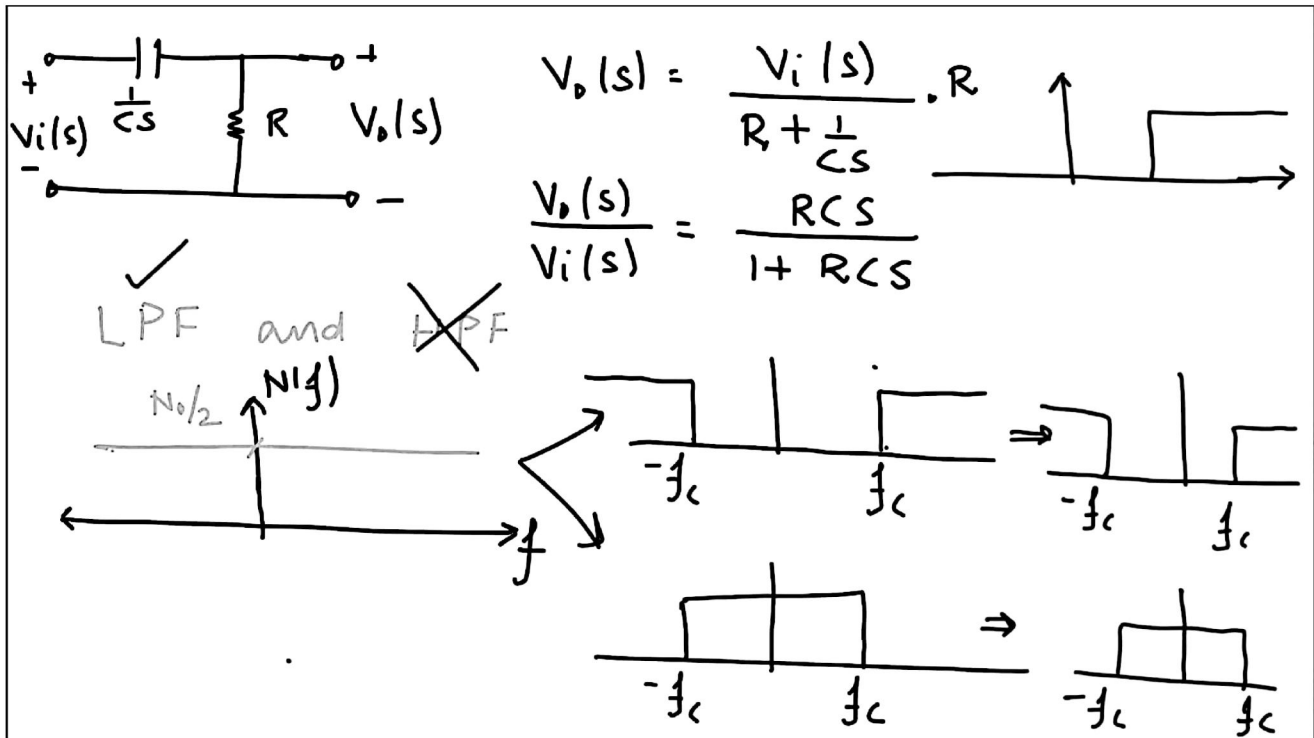

$$V_o(s) = \frac{V_i(s)}{\left[(1+s) \parallel \left(1 + \frac{1}{s}\right) \right] + \left(1 + \frac{1}{2s}\right)}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{2s+1}{2s}}{\frac{(1+s)\left(1 + \frac{1}{s}\right)}{1+s+1+\frac{1}{s}} + 1 + \frac{1}{2s}} = \frac{\frac{2s+1}{2s}}{1 \frac{1+s+1+\frac{1}{s}}{1+s+1+\frac{1}{s}} + 1 + \frac{1}{2s}}$$

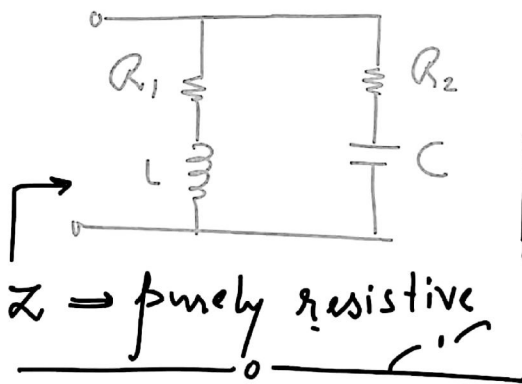
$$\boxed{\frac{V_o(s)}{V_i(s)} = \frac{2s+1}{4s^2+1}} \quad \text{Order} = \underline{\underline{1}}$$



This circuit will be at resonance at any freq. provided.

$$\boxed{R_1^2 = R_2^2 = \frac{L}{C}} \quad \checkmark$$


$Z =$ purely resistive

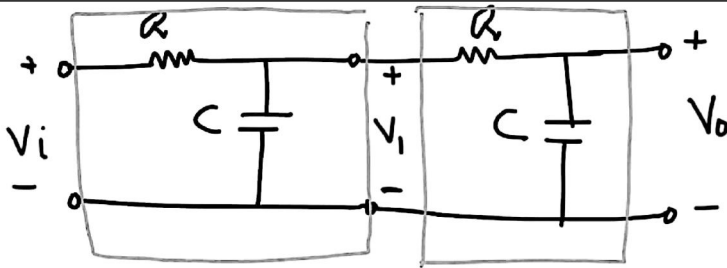

$$A_{V_1} = \frac{V_1}{V_i}$$

$$A_{V_2} = \frac{V_o}{V_1}$$
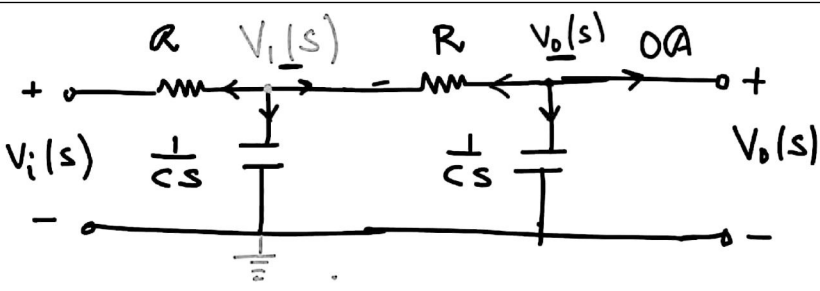
$$\begin{aligned}
 A_V &= A_{V_1} \cdot A_{V_2} \\
 &= \frac{1}{1+RCs} \cdot \frac{1}{1+RCs} \\
 &= \frac{1}{(1+RCs)^2} \\
 &= \frac{1}{R^2 C^2 s^2 + 2RCs + 1}
 \end{aligned}$$



$$\frac{V_o(s)}{V_i(s)} = ?$$

$$\frac{V_1(s) - V_i(s)}{R} + \frac{V_1(s)}{1/Cs} + \frac{V_1(s) - V_o(s)}{R} = 0$$

$$V_1(s) \left[\frac{1}{R} + Cs + \frac{1}{R} \right] = \frac{V_i(s)}{R} + \frac{V_o(s)}{R}$$

$$V_1(s) \left[\frac{2 + RCs}{R} \right] = \frac{V_i(s) + V_o(s)}{R}$$

$$V_1(s) = \frac{V_i(s) + V_o(s)}{2 + RCs} \quad \text{--- ①}$$

$$\frac{V_o(s) - V_1(s)}{R} + \frac{V_o(s)}{1/c s} = 0$$

$$V_o(s) \left[\frac{1}{R} + c s \right] = \frac{V_1(s)}{R}$$



$$V_o(s) \left[\frac{1 + RCs}{R} \right] = \frac{1}{R} \left[\frac{V_i(s) + V_o(s)}{2 + RCs} \right]$$


$$V_o(s) \left[(1 + RCs)(2 + RCs) \right] = V_i(s) + V_o(s)$$

$$V_o(s) \left[2 + RCs + 2RCs + R^2 c^2 s^2 - 1 \right] = V_i(s)$$

$$\boxed{\frac{V_o(s)}{V_i(s)} = \frac{1}{R^2 c^2 s^2 + 3RCs + 1}}$$

Aditya Kanwal Ex 1 es

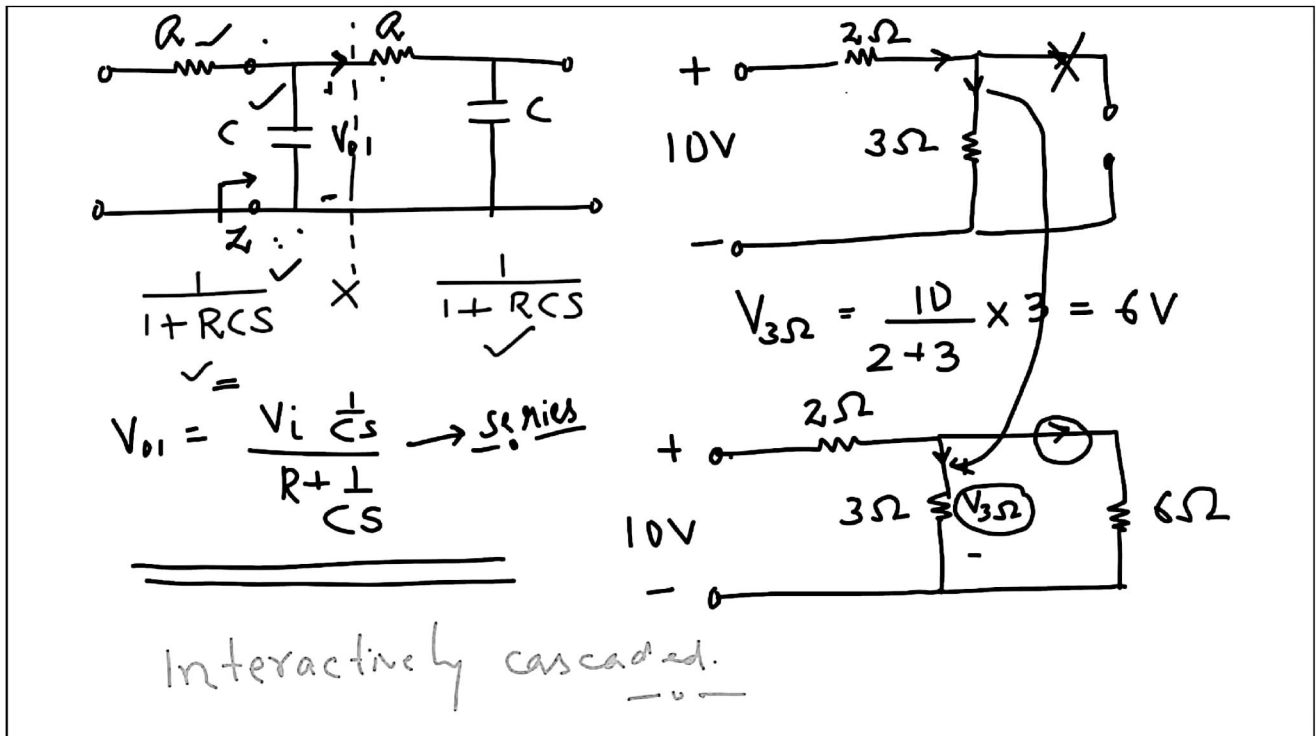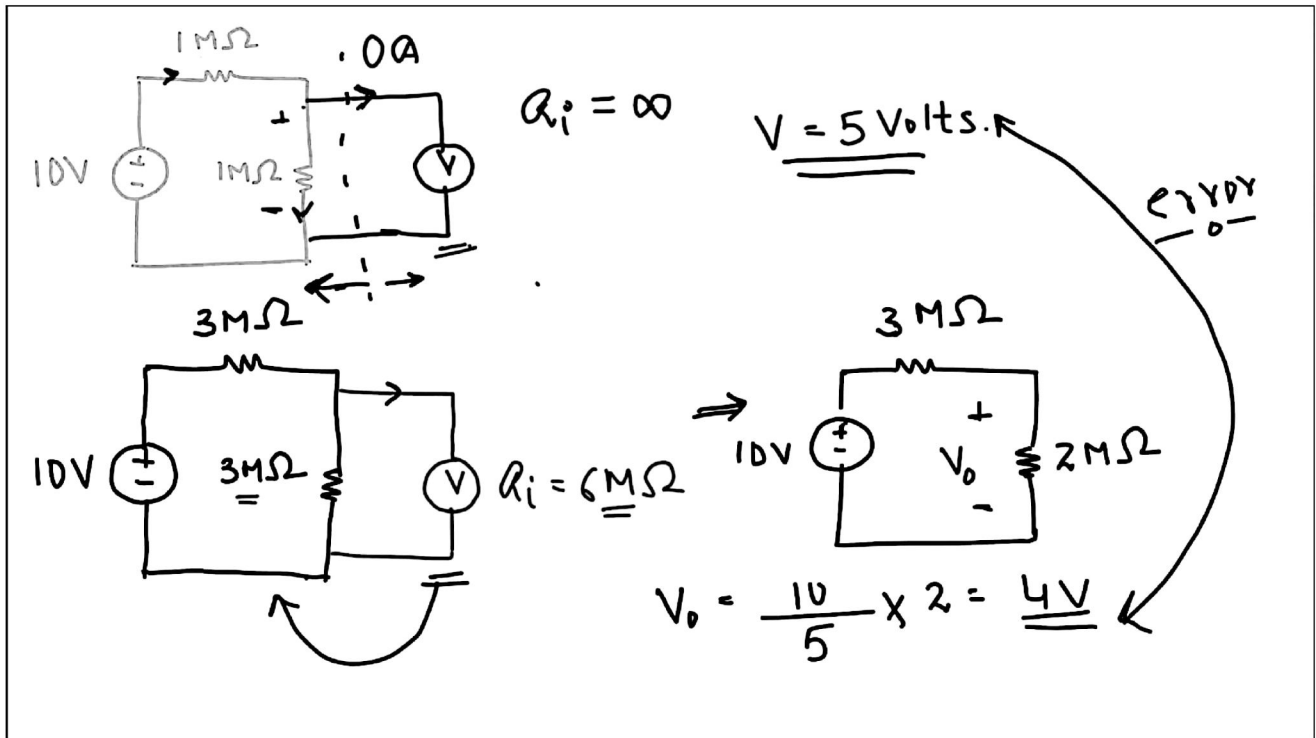

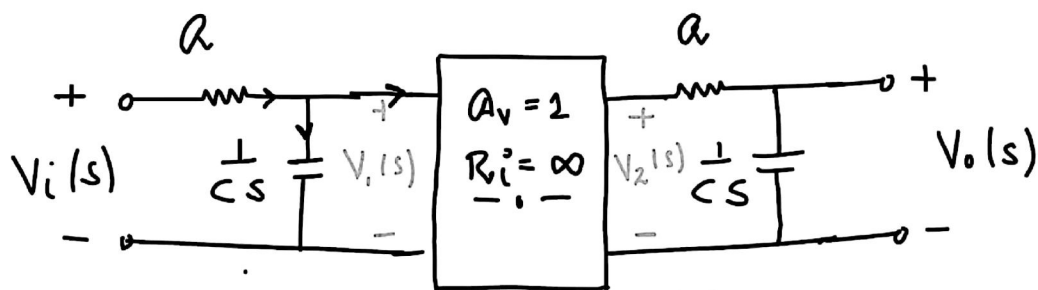


$$\begin{aligned} \frac{V_o(s)}{V_i(s)} &= \frac{V_o(s)}{V_2(s)} \cdot \frac{V_2(s)}{V_1(s)} \cdot \frac{V_1(s)}{V_i(s)} \\ &= \frac{\frac{1}{Cs}}{R + \frac{1}{Cs}} \cdot 1 \cdot \frac{\frac{1}{Cs}}{R + \frac{1}{Cs}} = \frac{1}{1 + RCs} \cdot \frac{1}{1 + RCs} \\ &= \frac{1}{(1 + RCs)^2} = \frac{1}{R^2 C^2 s^2 + 2RCs + 1} \end{aligned}$$

When \Rightarrow non-interactively cascaded.

$$A_v = A_{v_1} \cdot A_{v_2} \cdot A_{v_3} \dots$$

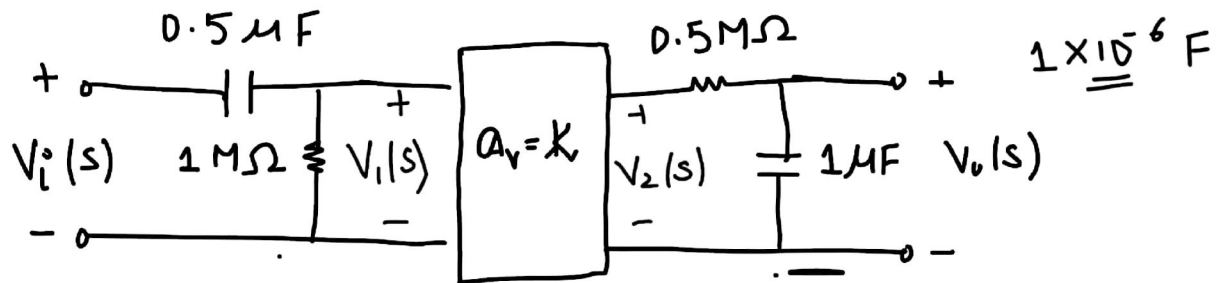$\rightarrow \frac{1}{s+1} \Rightarrow 2$ systems \Rightarrow non interactively cascade.
 \Rightarrow Final system T.F = ? $\frac{1}{s+1} \cdot \frac{1}{s+1} = \frac{1}{(s+1)^2}$



$$\frac{V_o(s)}{V_i(s)} = \frac{V_o(s)}{V_2(s)} \cdot \frac{V_2(s)}{V_1(s)} \cdot \frac{V_1(s)}{V_i(s)} \quad \frac{V_o(s)}{V_i(s)} = \frac{k(0.5s)}{(1+0.5s)^2}$$

$$= \frac{\frac{1}{5\mu}}{0.5\text{M} + \frac{1}{5\mu}} \cdot k \cdot \frac{1\text{M}}{1\text{M} + \frac{1}{0.5\mu\text{s}}} = \frac{1}{1+0.5s} \cdot k \cdot \frac{0.5s}{1+0.5s}$$

Ex:- Find the T.F of a system whose impulse response is $t e^{-t}$.

Sol₂ T.F = LT[IR] $\Rightarrow T(s) = C(s) = \frac{1}{(s+1)^2}$

Ex:- Find the T.F of a system whose step response is $t \cdot e^{-t}$.

Sol₂ $T(s) = \frac{C(s)}{R(s)} \quad C(s) = \frac{1}{(s+1)^2} \quad X(t) = u(t)$
 $R(s) = \frac{1}{s}$

$$T(s) = \frac{s}{(s+1)^2}$$