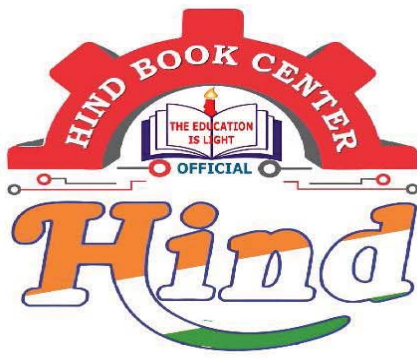




Hindbookcenter



Hind Book Center & Photostat


MADE EASY

**Electronics Engineering
Toppers Handwritten Notes
Analog Electronics
By- Iftaqar Ahmed Sir**

- Colour Print Out
- Blackinwhite Print Out
- Spiral Binding,& Hard Binding
- Test Paper For IES GATE PSUs IAS, CAT,SSC
- All Notes Available & All Book Availabie
- Best Quaity Handwritten Classroom Notes & Study Materials
- IES GATE PSUs IAS CAT Other Competitive/Entrence Exams

Visit us:-www.hindbookcenter.com

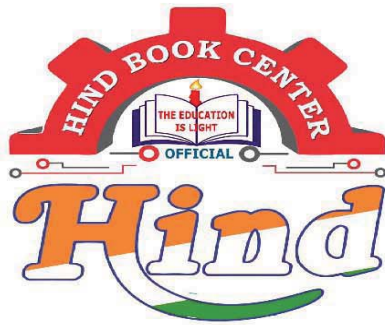**Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9711475393**



Hindbookcenter



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE
COURIERS SERVICE AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

ESE, GATE, PSUs BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

❖ IES –PRELIMS & MAINS

❖ GATE

➤ NOTE;- ALL ENGINEERING BRANCHS

➤ ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK
RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	---	--	--

Website: www.hindbookcenter.com

Contact Us: 9711475393

Gate: 10M to 12M

- ① Diode Circuits (2M to 3M)
- ② BJT circuits Biasing
Amplifier (2M-3M)
- ③ MOSFET circuits Biasing
Amplifiers
CMOS Inverter } 4M
- ④ Op-amp (2M-4M)
- ⑤ Other Topics
Multistage Amplifier
Feedback Amplifier
Oscillator, Differential Amplifier.

For ESE :-

ESE Prelims: 20M to 30M


ESE Mains: 100M

- ① JFET Biasing
Amplifier
- ② IC 555 (Timer IC)
- ③ Tuned Amplifier
+
Power Amplifier

Books:

- ① Microelectronic circuits
- Sedra & Smith
- ② Electronic Circuits
- Donald Neuman

BJT Circuits :

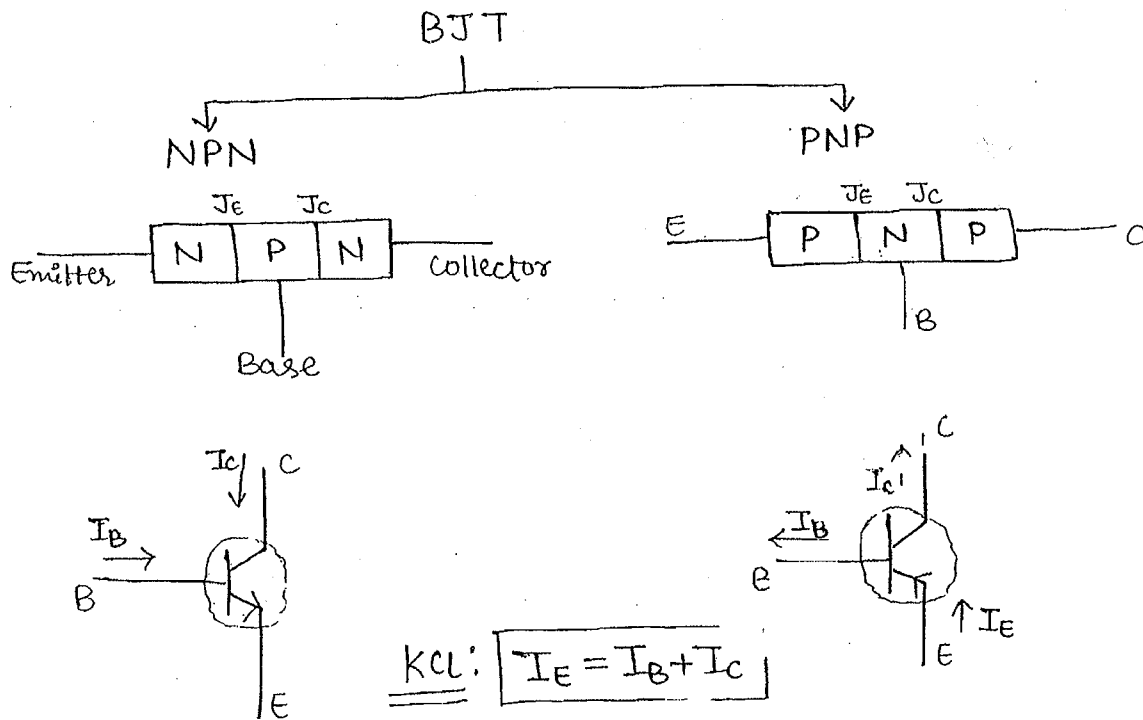

Region of operation	I_E	I_C	Application
① Cut-off	R.B.	R.B.	OFF Switch
② Saturation	F.B.	F.B.	ON Switch
③ Active Or Forward Active	F.B.	R.B.	Amplifier
④ Reverse Active	R.B.	F.B.	Attenuator,

⇒ BJT is not used in Reverse active region because BJT acts as Attenuator in Reverse Active mode. (Gain < 1)

Important Formulae -

$$① I_E = I_{ES} (e^{V_{BE}/V_T} - 1) \quad \text{for NPN}$$

$$I_E = I_{ES} (e^{V_{EB}/V_T} - 1) \quad \text{for PNP}$$

where, $I_{ES} \rightarrow$ Reverse saturation current in emitter junction (J_E)

$$I_{ES} \simeq \frac{Aq n_i^2 \times D_B}{w_B \times N_B}$$

, $I_{ES} \propto \text{Area of } J_E$

$$\boxed{I_E \propto \text{Area of } J_E}$$

$$D_B \begin{cases} D_P & \text{for PNP} \\ D_N & \text{for NPN} \end{cases}$$

, $w_B \rightarrow$ Base width

$N_B \rightarrow$ Doping conc. of base.

② If BJT is in Active Region

$$\therefore I_C = \alpha I_E + I_{CO} \simeq \alpha I_E$$

$$I_C = \beta I_B + (1 + \beta) I_{CO} \simeq \beta I_B$$

where,

$I_{CO} \rightarrow$ Reverse saturation current of J_C .
It is also negligible effect.

$\alpha \rightarrow$ common base current gain
($\alpha = \beta * \gamma$)

$\beta \rightarrow$ common emitter current gain

$$\boxed{\beta = \frac{\alpha}{1 - \alpha}}$$

or

$$\boxed{\alpha = \frac{\beta}{\beta + 1}}$$

$\therefore \alpha \simeq 1$

$\therefore \beta$ is large number

* β is a measure of amplification property of BJT.

* A large β indicates better amplification property.


$$\therefore I_C \simeq \alpha I_E, \quad I_C = \alpha I_{ES} (e^{V_{BE}/V_T} - 1)$$

$$\boxed{I_C = I_S (e^{V_{BE}/V_T} - 1)}$$

$$\therefore I_S = \alpha \times I_{ES}$$

$\downarrow$
Saturation current

BJT behaviour in a circuit :-

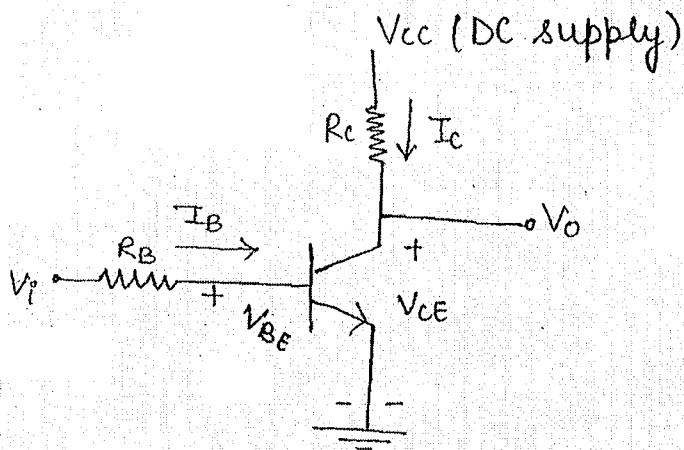

Let V_i be varied :-

- ① If $V_i < V_{BE}$ (cut in)
BJT remains OFF.

$$I_B = 0, I_C = 0$$

$$\therefore V_o = V_{CE} = V_{CC} - I_C R_C = V_{CC}$$

$$V_{BE}(\text{cut in}) \begin{cases} 0.6V \text{ for Si} \\ 0.1V \text{ for Ge} \end{cases}$$

- ② If $V_i > V_{BE}$ (cut in)
BJT starts conduction
i.e. I_B & I_C will flow.

$$\therefore \boxed{I_B = \frac{V_i - V_{BE}}{R_B}} \quad \boxed{I_C = \beta I_B}$$

$$\therefore \boxed{V_o = V_{CE} = V_{CC} - I_C R_C}$$

If $V_i \uparrow \rightarrow I_B \uparrow \rightarrow I_C \uparrow \rightarrow \text{Voltage drop in } R_C (I_C R_C) \uparrow \rightarrow V_{CE} \downarrow$

* V_{CE} can decrease upto V_{CEsat}

* V_{CEsat} is the minimum possible voltage which can appear b/w collector & emitter.

* V_{CE} can not become zero due to internal resistance of BJT.

$$V_{CEsat} \begin{cases} 0.2V \text{ for Si} \\ 0.1V \text{ for Ge} \end{cases}$$

* If V_{CE} becomes V_{CEsat} then it remains constant at V_{CEsat} . Hence, collector current (I_C) also becomes constant & BJT is said to be in saturation.
 If BJT enters in saturation, then,

$$V_{CE} = V_{CEsat}$$

& I_C remains constant at I_{Csat}

$$I_{Csat} = \frac{V_{CC} - V_{CEsat}}{R_C}$$

→ saturated collector current (I_C)
 OR
 maximum collector current (I_C)

* Base current (I_B) keeps increasing with V_i . Hence, BJT can not satisfy the relation $I_C = \beta I_B$ in saturation.

* In saturation, $\beta I_B > I_C$ or $I_C < \beta I_B$ or

$$I_B > \frac{I_{Csat}}{\beta}$$

* Emitter current (I_E) also keep increasing. Because

$$I_E = I_B + I_C$$

* Forced β :- It is the ratio of I_{Csat} & I_B , when BJT is in saturation.

$$\beta_{Forced} = \frac{I_{Csat}}{I_B}$$

If $V_i \uparrow \rightarrow I_B \uparrow \rightarrow \beta_{Forced} \downarrow$

$$\therefore \beta > \beta_{Forced}$$

* Overdrive (Degree of Saturation):

It is the ratio of normal β & forced β


$$\text{Overdrive} = \frac{\beta}{\beta_{\text{forced}}}$$

Overdrive is a measure of level of saturation.

overdrive = 1 $\Rightarrow$ onset (beginning) of saturation.


Overdrive > 1 $\Rightarrow$ weak saturation (or) soft saturation

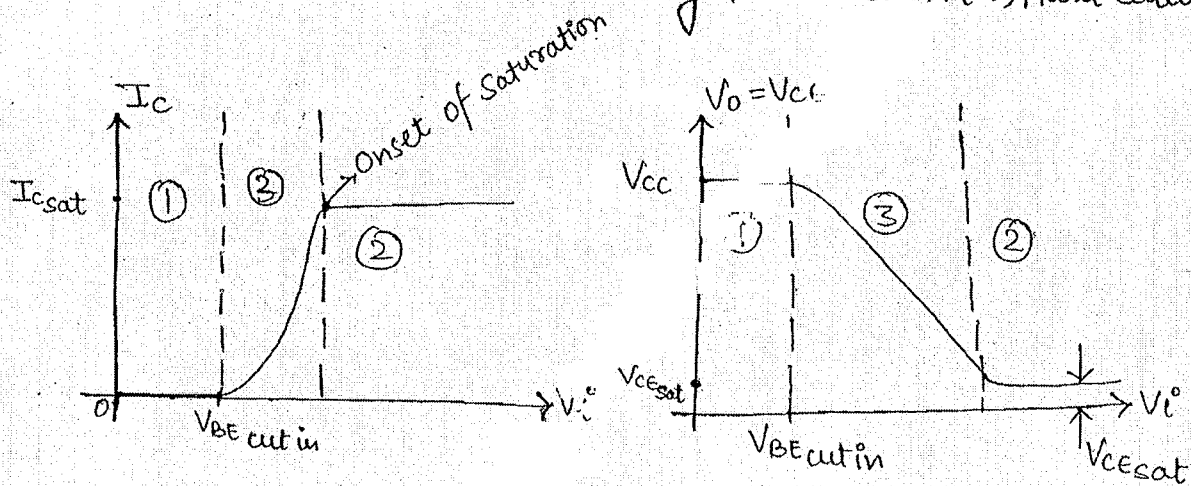Overdrive $\gg$ 1 $\Rightarrow$ Strong saturation (or) Hard saturation




$\Rightarrow$ Region ① is cut-off Region.
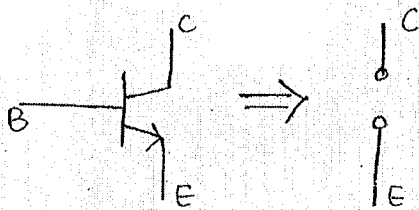
$$\left. \begin{array}{l} I_c = 0 \\ V_{CE} = V_{CC} \end{array} \right\} \text{open circuit OR OFF switch}$$



$\Rightarrow$ Region ② is saturation region, where I_c remains constant w.r.t. V_i
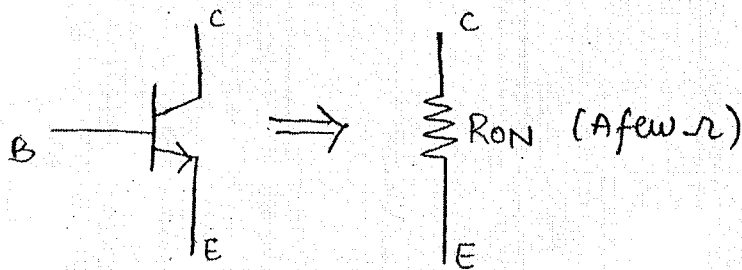
$$\left. \begin{array}{l} I_c = I_{c\text{sat}} \\ V_{CE} = V_{CE\text{sat}} \end{array} \right\} \text{ON switch}$$



$R_{ON} \Rightarrow$ ON resistance of BJT.

$$R_{ON} = \frac{V_{CEsat}}{I_{Csat}}$$

- $\Rightarrow$ Region (3) is active region, where collector current (I_C) varies with input voltage (V_i)
- $\rightarrow$ A BJT is said to be active if collector current (I_C) changes acc. to input voltage (V_i)
- $\rightarrow$ If BJT is used as small signal amplifier then it is operated in active region, so that small changes in input can create proportionate change in I_C .

Procedure to Check Operating Region of BJT.

Method 1:

- ① Assume BJT in saturation


$$V_{CE} = V_{CEsat} \begin{cases} 0.2V \text{ for Si} \\ 0.1V \text{ for Ge} \end{cases}$$

- ② Calculate I_B and I_C or I_{Csat}

- ③ Calculate minimum base current required to operate in BJT in saturation (I_{Bmin})

$$I_{Bmin} = \frac{I_{Csat}}{\beta}^*$$

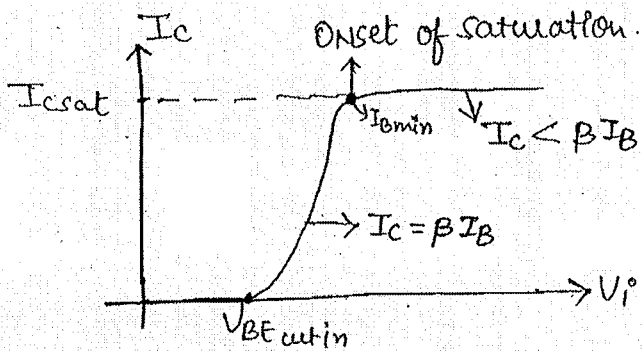$\rightarrow$ Base current at onset of saturation.



④ Compare I_B and I_{Bmin} .

If $I_B \geq I_{Bmin} \Rightarrow$ BJT is in saturation region.



If $I_B < I_{Bmin} \Rightarrow$ BJT is in active region.

Que- In circuit shown BJT has $\beta = 100$, $V_{CEsat} = 0.2V$ and $V_{BEsat} = 0.8V$, find,

① operating region if $R_c = 2K$, $R_B = 80K$

② If $R_c = 1K$, then find the value of R_B such that BJT remains in saturation.

Sol:- $\because V_i = 3V$

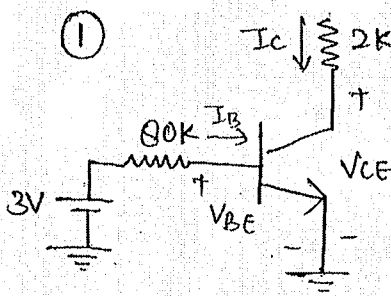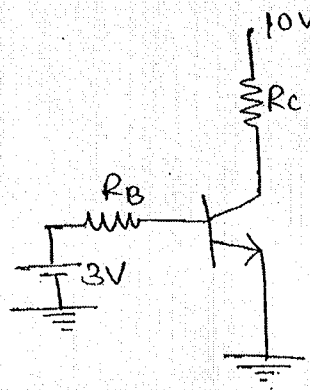

let Assume BJT in saturation

$$V_{CE} = 0.2V$$

$$V_{BE} = 0.8V$$

$$\therefore I_B = \frac{3 - V_{BE}}{80} = \frac{2.2}{80} = \underline{\underline{0.0275\ mA}}$$

$$I_C = I_{Csat} = \frac{10 - V_{CE}}{2} = \frac{9.8}{2} = \underline{\underline{4.9\ mA}}$$